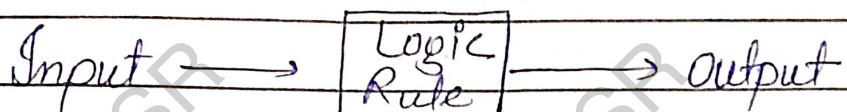




\* Logic Gate :-

Logic gate is a digital device or circuit which take some input and give suitable output using suitable logic rule.



\* In logic gate world we use two digit they are 0 and 1.


0 means → off, False, No, Low, disable

1 means → on, True, Yes, High, enable

\* Truth Table (TT) :-

The tabular representation of possible input and output.

Classification of logic gate :-

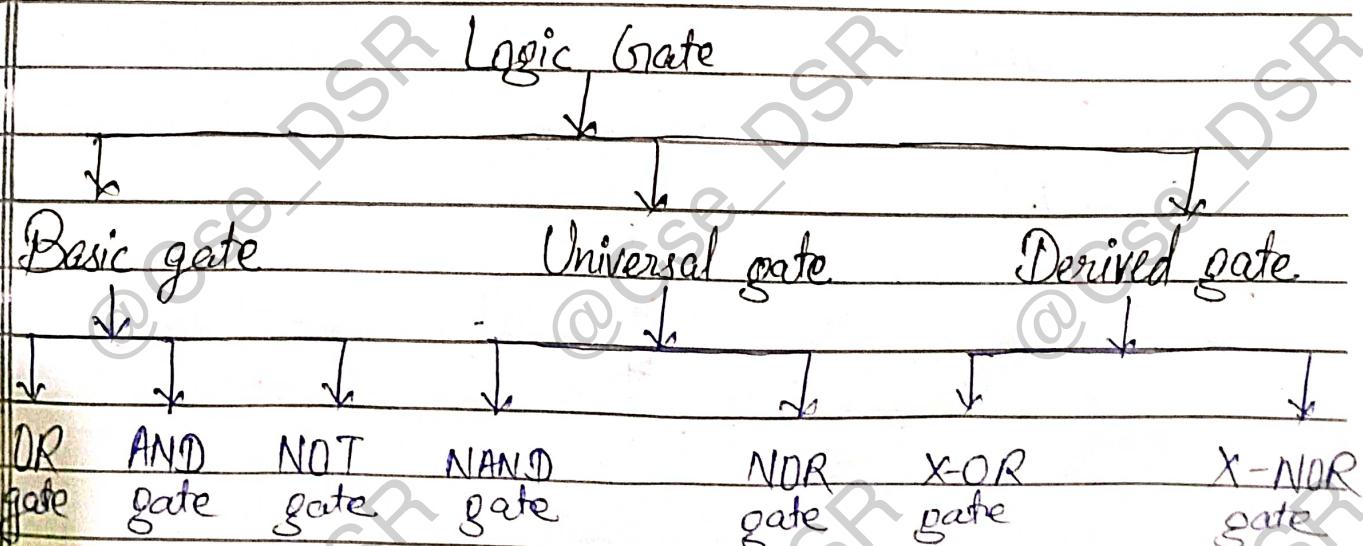


## \* Logic gate operator :-

- OR operator  $\rightarrow (+)$
- AND operator  $\rightarrow (\cdot)$
- NOT operator  $\rightarrow (\bar{A})$

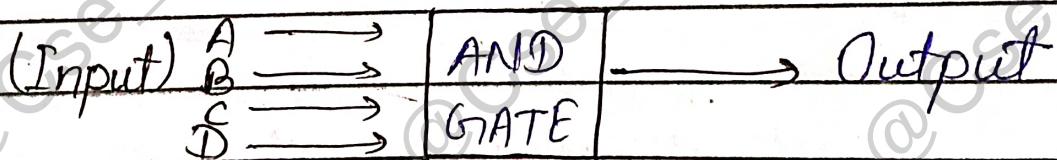
### 1) AND GATE :-

- It is a type of basic gate.
- It has many input and one output.
- If we give  $A, B, C, \dots$  in the input then we get  $A \cdot B \cdot C \dots$  in the O/P.
- Here, dot ( $\cdot$ ) means ANDing.
- If we assume input as a switch then ANDing means all switch connected in series.




Symbol !—

I/P :-

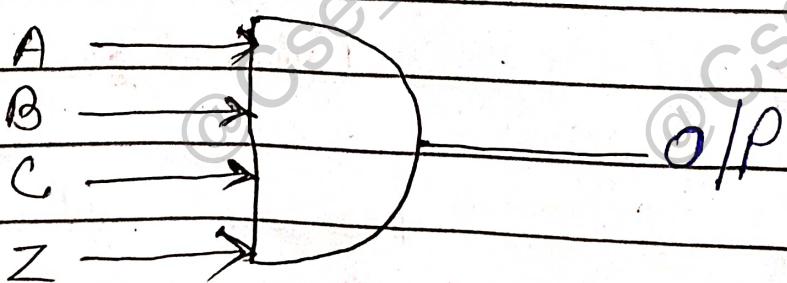


Two input AND gate :-

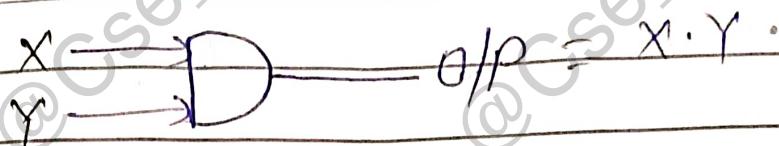

Truth Table

Circuit Diagram

Input		Output
X	Y	$X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

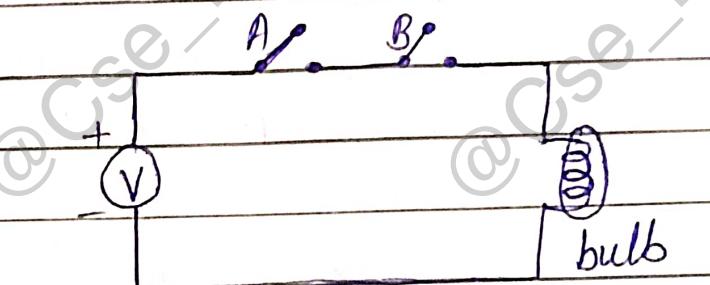

OR GATE :-


It is a type of basic gate.

It has many input and one output.

If we give A, B, C, ... in the input then we get  
 $A + B + C + \dots$  in the output.


Here plus (+) sign indicate all input act as a switch and they are connected in parallel.

Symbols :-

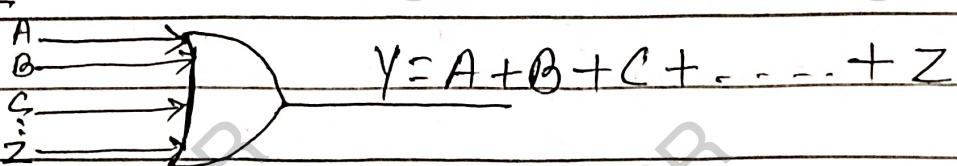

$$Y = A + B + C + \dots + Z$$


Two input OR gate :

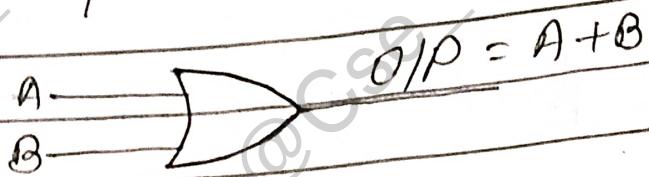

Truth Table

Circuit Diagram


Input	Output	
A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

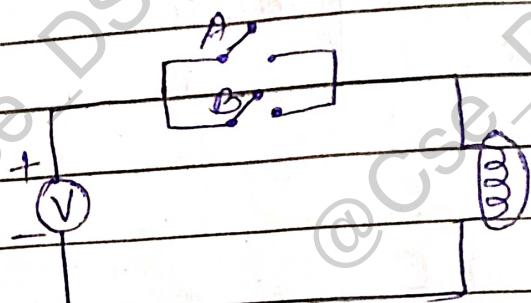

3) NOT GATE :-


- It is the type of basic gate.
- It has one input and one output.
- If we give A in the input then we get  $\bar{A}$  in the output.
- The main work of this logic gate to invert the input.
- So, NOT gate is also called INVERTER.

Symbol :-

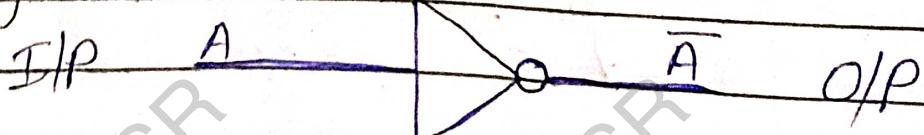

Truth Table

Input	Output
A	$\bar{A}$
0	1
1	0

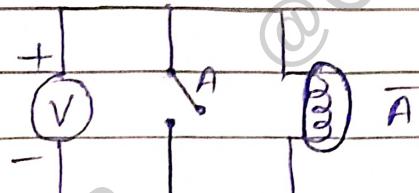Circuit Diagram\* Basic Gate :-

→ AND, OR and NOT gates are called basic gate.

→ These gates are called basic gate because all logic circuit made by help of these logic gate.

\* Universal Gate :-

→ By the help of NAND gate and NOR gate, we can make every type of logic gate and logic circuit.

4) NAND Gate :-


→ It is the type of universal gate.

→ It is the combination of two basic logic gate.

They are NOT gate and AND gate..

→ It has many input and one output.

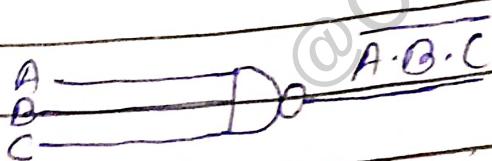
If we give  $A, B, C$  in the input then  
we get  $\overline{A \cdot B \cdot C}$  in the output.



Truth Table

Input	Output	
A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

Circuit Diagram

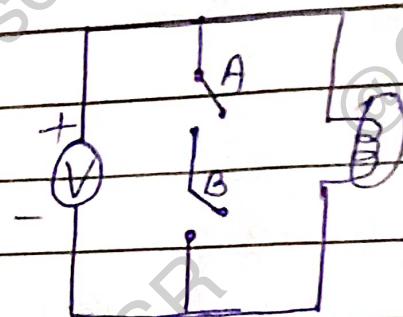

### 5) NOR Gate :-


It is the type of universal gate.  
It is the combination of two basic logic gates.  
They are NOT gate and OR gate.  
It has many input and one output.  
If we give  $A, B, C$  in the input, then  
we get  $\overline{A + B + C}$  in the output.



Truth Table

Circuit Diagram

Input	Output	$A + B$
A	B	
0	0	1
0	1	0
1	0	0
1	1	0

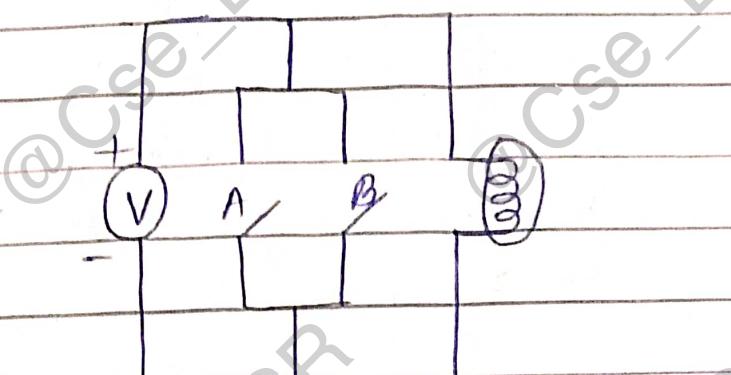

X-OR, Exclusive OR, Ex-OR :-

It is the type of special gate.


It is the combination of AND, OR and NOT.

If we give A, B in the input then we get  
 $\bar{A}B + A\bar{B}$ .

$\bar{A}B + A\bar{B}$  is written as  $A \oplus B$

$$\text{i.e., } \bar{A}B + A\bar{B} = A \oplus B$$


Symbol:-

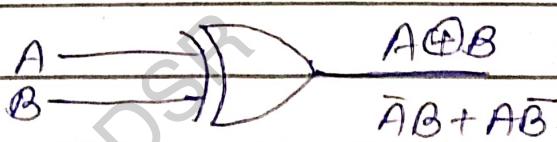

Truth Table


A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

Circuit Diagram

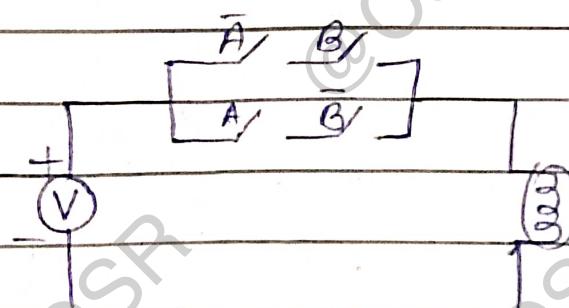

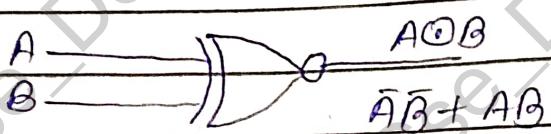7) X-NOR, Exclusive NOR, Ex-NOR :-


- It is the type of special gate.
- It is the combination of AND, OR and NOT.
- If we give  $A, B$  in the input then we get  $\bar{A}\bar{B} + A\bar{B}$ .
- $\bar{A}\bar{B} + A\bar{B}$  is written as  $A \oplus B$ .  
i.e.,  $\bar{A}\bar{B} + A\bar{B} = A \oplus B$       ↑ Exclusive NOR



Truth Table

Circuit Diagram


A	B	$A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

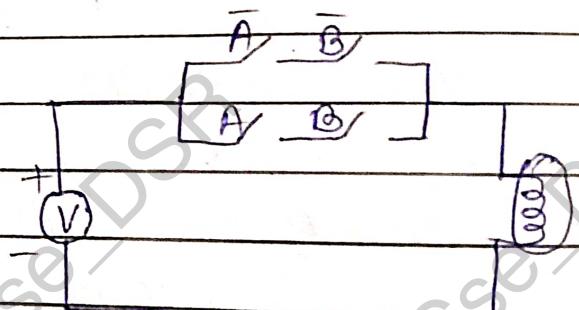

H.W.

$$① Y = \overline{(A+B)C + D}$$

$$② Y = \overline{\bar{A}B + \bar{A}C}$$

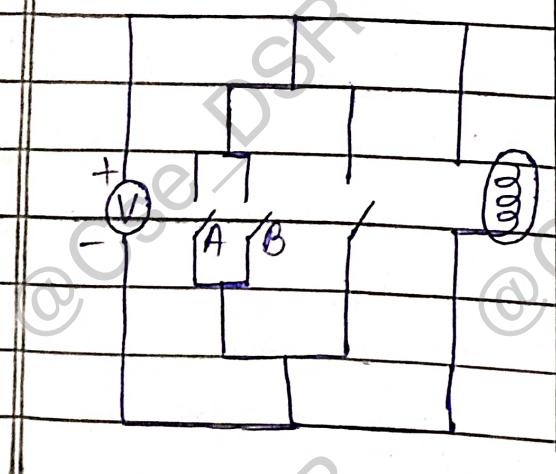



Note:-

i) To make any equivalent electrical circuit, we should mind the followings:-

a) If given expression is  $A \cdot B$ , then both are connected in a series and it connect with bulb in series also.

b) If expression is  $\overline{A \cdot B}$ , then both will be connected in series with each other and whole will be connected in parallel with bulb.

ii)

a) If expression is  $A + B$ , then it will be connected to each other in parallel and whole will be connected with the bulb in series.

If expression is  $\overline{A + B}$ , then it will be connected to each other in parallel and whole will be connected with bulb in parallel also.

## \* De-Morgan's Theorem :-

It states that :-

- i) The complement of sum is equal to product of complements.  
i.e,

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

- ii) The complement of product is equal to sum of complements.  
i.e,

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

## # Proof (Using truth table):-

A	B	$\overline{A}$	$\overline{B}$	$A \cdot B$	$A+B$	$\overline{A \cdot B}$	$\overline{A+B}$	$\overline{A}+\overline{B}$	$\overline{A} \cdot \overline{B}$
0	0	1	1	0	0	1	1	1	1
0	1	1	0	0	1	1	0	1	0
1	0	0	1	0	1	1	0	1	0
1	1	0	0	1	1	0	0	0	0

Now, from above that table, it is clear  
that

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

$$\text{and } \overline{A \cdot B} = \overline{A} + \overline{B}$$

Proved


## # Proof - II (Using gate)

$$1. \quad A + B = \bar{A} \cdot \bar{B}$$

LHS =  $\overline{A + B}$



$$\text{RHS} = \bar{A} \cdot \bar{B}$$

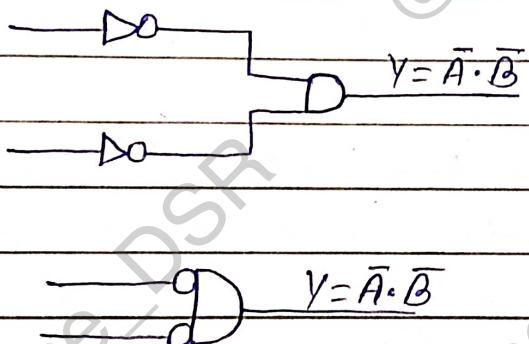



From the above decision, it is clear that NOR gate is replaced by inverted AND gate, that is negative AND gate.

$$2. \quad A \cdot B = \bar{\bar{A}} + \bar{\bar{B}}$$

LHS =  $\overline{A \cdot B}$



$$RHS = \bar{A} + \bar{B}$$

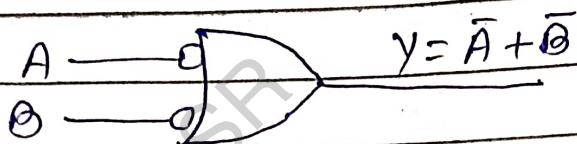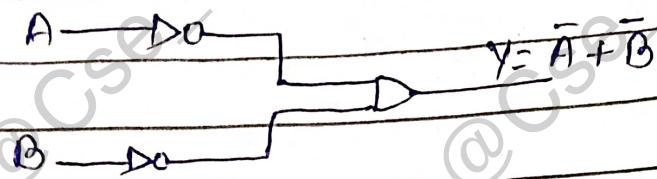

NAND gate can be replaced by negative OR gate or inverted OR gate.

Q. Prove that  $AB + \bar{A}C = AB + \bar{A}C + BC$   
{this is known as consensus theorem}

$$RHS = AB + \bar{A}C + BC$$

multiplying by  $(A + \bar{A})$  into  $BC$

$$= AB + \bar{A}C + BC(A + \bar{A})$$

$$= AB + \bar{A}C + ABC + \bar{A}BC$$

$$= AB + ABC + \bar{A}C + \bar{A}BC$$

we know that

$$1 + C = 1$$

$$\text{and } 1 + \bar{C} = 1$$

$$\Rightarrow AB(1) + \bar{A}C(1)$$

$$= AB + \bar{A}C = LHS$$

Proved



DATE: \_\_\_/\_\_\_/\_\_\_

PAGE: \_\_\_

2<sup>nd</sup> proof :-

$$\text{LHS} = AB + \bar{A}C$$

Now, multiplying the  $AB$  with  $(I+C)$   
and  $\bar{A}C$  with  $(I+B)$

$$= AB(I+C) + \bar{A}C(I+B)$$

$$= AB + A\bar{B}C + \bar{A}C + \bar{A}BC$$

$$= AB + \bar{A}C + ABC + \bar{A}BC$$

$$= AB + \bar{A}C + BC(A + \bar{A})$$

$$= AB + \bar{A}C + BC(1) \quad \{ \because A + \bar{A} = 1 \}$$

$$= AB + \bar{A}C + BC = \text{RHS}$$

Proved

Q. Prove that  $AB + A\bar{B}\bar{C} + A\bar{B}D = AB$   
(Redundancy theorem)

$$\text{LHS} = AB + A\bar{B}\bar{C} + A\bar{B}D$$

$$= AB(1 + \bar{C} + D)$$

$$= AB(1 + D)$$

$$= AB = \text{RHS}$$

Proved

Q. Prove that :-

$$\text{(i)} \quad A \oplus B = \overline{A \oplus B}$$

$$\text{(ii)} \quad \overline{A \oplus B} = \bar{A} \oplus \bar{B} = A \oplus \bar{B}$$

$$\text{(iii)} \quad A \bar{B} + B = A + B$$

$$\text{(iv)} \quad B \oplus (B \oplus A C) = A C$$

$$\text{(v)} \quad A \oplus B = \bar{A} \oplus \bar{B}$$

Some formulae :-

For XOR gate :-

$$\textcircled{1} \quad A \oplus A = 0$$

$$\textcircled{2} \quad A \oplus \bar{A} = 1$$

$$\textcircled{3} \quad A \oplus 1 = \bar{A}$$

$$\textcircled{4} \quad A \oplus 0 = A$$

For XNOR gate :-

$$\textcircled{1} \quad A \odot A = 1$$

$$\textcircled{2} \quad A \odot \bar{A} = 0$$

$$\textcircled{3} \quad A \odot 1 = A$$

$$\textcircled{4} \quad A \odot 0 = \bar{A}$$

$$\textcircled{1} \quad 1 + A = 1$$

$$\textcircled{2} \quad 1 + \bar{A} = 1$$

$$\textcircled{3} \quad A + \bar{A} = 1$$

(a) Prove that :-

$$(a) A \oplus B = \overline{A \odot B}$$

$$\text{LHS} = A \oplus B$$

$$= \bar{A}B + A\bar{B}$$

$$\text{RHS} = \overline{A \odot B}$$

$$= \overline{\bar{A}\bar{B}} + \overline{AB}$$

$$= \bar{A}\bar{B} \cdot \bar{A}\bar{B} \quad (\text{using DeMorgan's theorem})$$

$$= (\bar{A} + \bar{B}) \cdot (\bar{A} + \bar{B})$$

$$= (A + B) \cdot (\bar{A} + \bar{B})$$

$$= A\bar{A} + A\bar{B} + \bar{A}B + B\bar{B}$$

$$= 0 + A\bar{B} + \bar{A}B + 0$$

$$= A\bar{B} + \bar{A}B$$

$$= \text{LHS}$$

Proved

(b)  $A\bar{B} + B = A + B$

$$\text{LHS} = A\bar{B} + B$$

$$= A\bar{B} + B(1+A)$$

$$= A\bar{B} + AB + B$$

$$= A(B + \bar{B}) + B$$

$$= A + B$$

$$= \text{RHS}$$

Proved

(C)

$$A \oplus B = \bar{A} \oplus \bar{B}$$

$$LHS = A \oplus B$$

$$= \bar{A}B + A\bar{B}$$

$$RHS = \bar{A} \oplus \bar{B}$$

$$= \bar{\bar{A}}\bar{B} + \bar{A}\bar{\bar{B}}$$

$$= A\bar{B} + \bar{A}B$$

$$= LHS \quad \underline{\text{Proved}}$$

(d)

$$\overline{A \oplus B} = \bar{A} \oplus B = A \oplus \bar{B}$$

$$LHS = \overline{A \oplus B}$$

$$= \overline{\bar{A}B + A\bar{B}}$$

$$= (\bar{A} + \bar{B}) \cdot (\bar{A} + B)$$

$$= (A + \bar{B}) \cdot (\bar{A} + B)$$

$$= A \cdot \bar{A} + A\bar{B} + \bar{A}B + B \cdot \bar{B}$$

$$= 0 + AB + \bar{A}\bar{B} + 0$$

$$= AB + \bar{A}\bar{B}$$

$$RHS_1 = \bar{A} \oplus B$$

$$= \bar{A}B + \bar{A}\bar{B}$$

$$= AB + \bar{A}\bar{B} = LHS$$

$$RHS_2 = A \oplus \bar{B}$$

$$= \bar{A}\bar{B} + A\bar{\bar{B}}$$

$$= AB + \bar{A}\bar{B} = LHS = RHS_1$$

$$\text{Hence, } LHS = RHS_1 = RHS_2$$

Proved

$$(e) B \oplus (A \oplus AC) = AC$$

1<sup>st</sup> proof! —

$$\begin{aligned} LHS &= B \oplus A \oplus AC \\ &= 0 \oplus AC \\ &= AC \end{aligned}$$

$$= RHS$$

Proved

2<sup>nd</sup> proof! —

$$\begin{aligned} LHS &= B \oplus (A \oplus AC) \\ &= \bar{B}(A \oplus AC) + B(\overline{A \oplus AC}) \\ &= \bar{B}(\bar{B}AC + B\bar{AC}) + B(\bar{B}AC + B\bar{AC}) \\ &= A\bar{B}C + \bar{B}B\bar{AC} + B(\bar{B}AC \cdot B\bar{AC}) \\ &= A\bar{B}C + 0 + B(1\bar{B} + \bar{AC}) \cdot (\bar{B} + \bar{AC}) \\ &= A\bar{B}C + B(1(A + \bar{AC})) \cdot (\bar{B} + AC) \\ &= A\bar{B}C + B(A\bar{B} + A\bar{AC} + B\bar{AC} + 0) \\ &= A\bar{B}C + B(0 + A\bar{B}C + \bar{B}\bar{AC} + 0) \\ &= A\bar{B}C + A\bar{B}C + 0 \\ &= AC(\bar{B} + B) \\ &= AC \\ &= RHS \end{aligned}$$

Proved

\* Minimize the given function :-

$$\begin{aligned} i) \quad Y &= \overline{ABC} + \overline{A}\overline{BC} + AB + \overline{AC} \\ &= \overline{ABC} \cdot \overline{A}\overline{BC} + AB + \overline{AC} \\ &= \overline{ABC} \cdot A\overline{B}\overline{C} + AB + (\bar{A} + \bar{C}) \\ &= (\bar{A} + \bar{B} + \bar{C}) \cdot \{\bar{A} + \bar{B} + \bar{C}\} + AB + (\bar{A} + \bar{C}) \\ &= (\bar{A} + \bar{B} + \bar{C}) \cdot (A + \bar{B} + \bar{C}) + AB + \bar{A} + \bar{C} \\ &= 0 + \overline{AB} + \bar{A}\bar{C} + A\bar{B} + \overline{B} + \overline{B}\bar{C} + A\bar{C} + \overline{B}\bar{C} + \bar{C} \\ &\quad + A\bar{B} + \bar{A} + \bar{C} \\ &= \bar{A}\bar{B} + \bar{A}\bar{C} + A\bar{B} + \bar{B} + A\bar{C} + \bar{B}\bar{C} + \bar{C} + AB + \bar{A} \\ &= \bar{A}\bar{B} + \bar{A}\bar{C} + \bar{A} + A\bar{B} + \bar{B} + \bar{B}\bar{C} + A\bar{C} + \bar{C} + AB \\ &= \bar{A} + \bar{B} + \bar{C} + AB \\ &= \bar{A}(1 + B) + B + \bar{C} + AB \\ &= \bar{A} + \bar{A}B + AB + \bar{B} + \bar{C} \\ &= \bar{A} + B(A + \bar{A}) + \bar{B} + \bar{C} \\ &= \bar{A} + \bar{B} + \bar{C} + B \\ &= \bar{A} + \bar{C} + (\bar{B} + B) \\ &\stackrel{S}{=} \bar{A} + \bar{C} + 1 \\ &= 1 \end{aligned}$$

\* SOP formed expression (Sum of Product):

Any boolean function is ORed of individual ANDed terms then that function is said to be in SOP form.

Ex:-

$$Y = AB + AC + AC + A\bar{C}$$

\* POS formed expression (Product of sum):

Any boolean function is ANDed of individual ORed terms then that function is said to be in POS form.

Ex:-

$$Y = (A + B)(B + C)(A + C)(B + \bar{C})$$

\* Standard form:— If any function containing all variables in each term then that function is said to be in standard form.


Q. Convert the given expression into standard SOP form:

1.  $Y = AB + BC + AC$

$$= AB(C + \bar{C}) + BC(A + \bar{A}) + AC(B + \bar{B})$$

$$= ABC + ABC + A\bar{B}C + A\bar{B}C + A\bar{B}C + A\bar{B}C$$
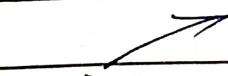
$$= ABC + A\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC.$$



This is the standard SOP form.



DATE: / /

PAGE: \_\_\_\_\_

- B. Convert the given expression into standard POS form:-

$$\begin{aligned}1. \quad Y &= (A+B)(B+C)(A+C) \\&= (A+B+C\bar{C})(A\bar{A}+B+C)(A+B\bar{A}+C) \\&= (A+B+C)(A+B+\bar{C})(A+B+C)(\bar{A}+B+C)(A+\bar{B}+C)(A+\bar{B}+\bar{C}) \\&= (A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(\bar{A}+B+C)\end{aligned}$$

This is the standard POS form.

Formula:-  $A+B+C\bar{C} = (A+B+C)(A+B+\bar{C})$

\* Min term, Max term & Don't care term

\* Min term:-

Each term present in standard SOP form expression is known as min term. That means output for each min term is 1. It is represented by

$$\sum_m ( ) \text{ or, } \sum_m l ( ).$$

\* Max term :-

Each term present in standard POS form expression is known as max term. That means output for each max term is 0. It is represented by  $\prod_M$

\* Don't care term :-

For any contradictory statement or any missing condition output may be represented as don't care term or it may be term as 0 or 1 for any truth table. It is denoted by d, x,

$$\sum_d x$$

- Q. Represent the given function in term of min term, max term and dont care term.

$$Y = A\bar{B}C + A\bar{B}C + A\bar{B}\bar{C} + AB\bar{C}$$

001	101	100	111
-----	-----	-----	-----

	ABC	Y
0	000	0
1	001	1
2	010	0
3	011	0
4	100	1
5	101	1
6	110	0
7	111	1

Min term :-

$$\sum_m (1, 4, 5, 7)$$

Max term :-

$$\prod_M (0, 2, 3, 6)$$

Q. Find the expression for given logic term:

4 person Ali, Bil, Charli, Donald may fight  
with certain conditions:-

- i) Ali can fight with anyone, if someone is watching.
- ii) Bil can fight with Charli, if no one is watching.
- iii) Charli can fight with anyone, if no one is watching.
- iv) Donald never start fighting.

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	x
0	1	0	1	1
0	1	1	0	0
0	1	1	1	x
1	0	0	0	0
1	0	0	1	x
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Min term :-

$$\sum_m (3, 6, 10, 11, 13, 14, 15)$$

$$\sum_d (15, 20)$$

Max term :-

$$\prod_M (0, 1, 2, 4, 8, 12) +$$


$$\sum_d (5, 7, 9)$$

## \* Karnaugh Map (K-Map)

K-map is the graphical representation of boolean function by which we can minimize any boolean function.


\* Two variable K-map :-

Q.1.  $y = \sum_m (0, 2, 3)$

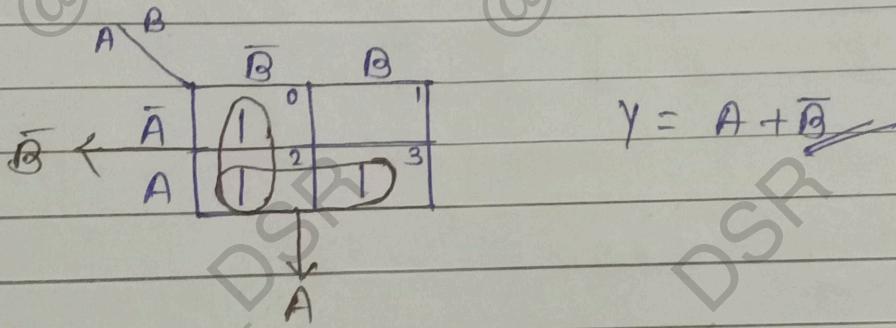


$$y = A + \bar{B}$$

Q.2.  $y = \sum_m (0, 1, 3)$

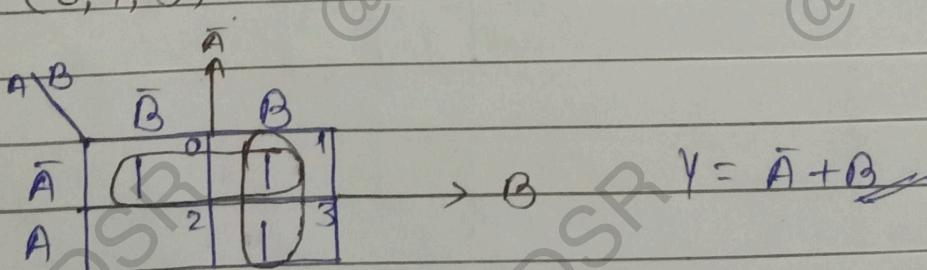

$$y = \bar{A} + B$$

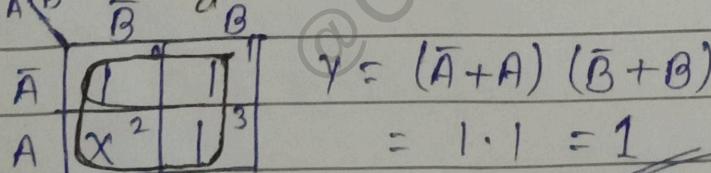Q.3.  $y = \sum_m (0, 1, 3) + \sum_m (2)$



$$y = (\bar{A} + A)(\bar{B} + B)$$

$$= 1 \cdot 1 = 1$$

Q.4.  $y = \sum_m (1, 2) + \sum_d (0)$

$A$	$B$	$\bar{B}$	$B$
$\bar{A}$	$X$	0	D
A	1	2	3

$$y = \bar{A} + \bar{B}$$

Q.5.  $y = \sum_m (0, 3)$

$A$	$B$	$\bar{B}$	$B$
$\bar{A}$	1	0	1
A	2	1	3

$$y = \bar{A}\bar{B} + AB$$

Q.6.  $y = \sum_m (1, 2)$

$A$	$B$	$\bar{B}$	$B$
$\bar{A}$	0	1	1
A	2	1	3


$$y = \bar{A}B + A\bar{B}$$

\* Steps :-

i) Divide the big sequence box into 4 equal parts.

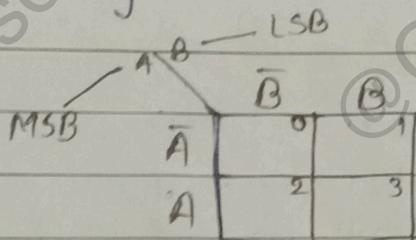ii) Let AB are two variables where A is MSB and B is LSB.

Separate these two variables into two parts. Write MSB (i.e. A) vertically and LSB (i.e. B) horizontally.



iii) Place 1 for each <sup>min</sup> term, X for don't care terms and for max term keep blank the respective box.

iv) For grouping purpose, try to make a group of four once. If not then two once, if not then individual and write its expression.

	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$	
$\bar{B}$	0	1	3	2	
$\bar{A}$	4	5	7	6	
A					

Q.  $y = f(A, B, C) = \sum_m (0, 1, 3, 5, 6, 7) + \sum_d 2$

$A \backslash BC$	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	$BC$
$\bar{A}$	0	1	3	X
A	4	1	5	7
				6

$$y = \bar{A} + B + C$$

Q.  $y = f(A, B, C) = \sum_m \text{all odd no.} + \sum_d 0, 2$

$A \backslash BC$	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	$BC$
$\bar{A}$	X	0	1	3
A	4	1	5	7
				6


$$y = C$$

Q.  $y = \sum_m \text{all even no.} + \sum_d 0, 3$

$A \backslash BC$	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	$BC$
$\bar{A}$	X	0	1	2
A	1	5	7	6


$$y = \bar{C}$$

Q.  $y = \sum_m (2, 4) + \sum_d 0, 3$

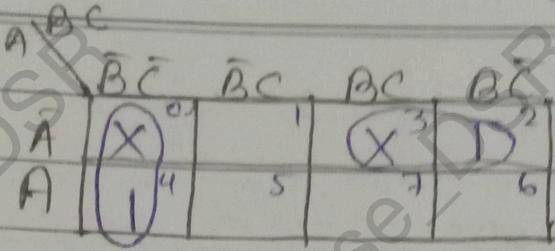


$$Y = B + \bar{B}C$$

Q.  $Y = \sum_m (0, 1, 2, 3, 4, 5, 6)$

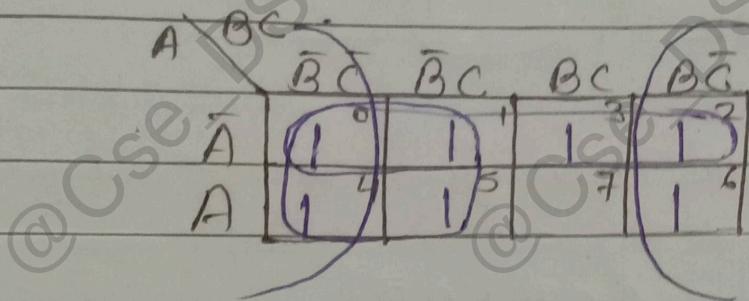

$$Y = \bar{A} + \bar{B} + \bar{C}$$

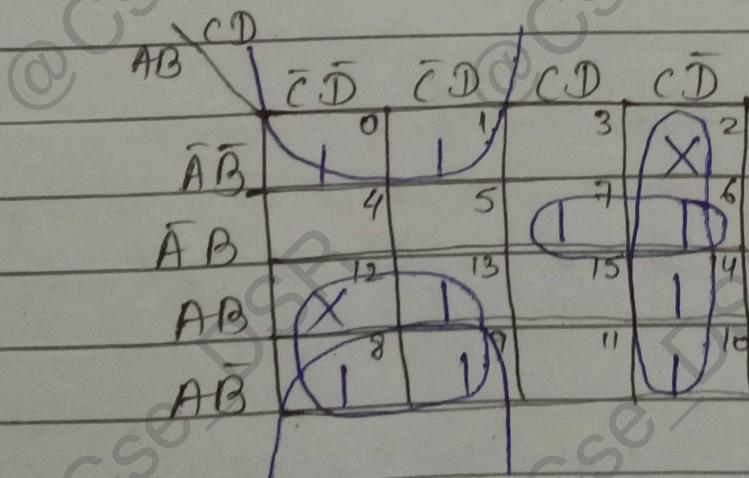Q.  $Y = \sum_i (0, 1, 6, 7, 8, 9, 10, 13, 14) + \sum_d (2, 12)$



$$Y = \bar{B}\bar{C} + A\bar{C} + C\bar{D} + \bar{A}BC$$

$$Y = \sum_m (\text{all odd m's}) + \sum_d 0, 2, 4, 6, 8, 10$$

$AB\backslash CD$	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$	X <sup>0</sup>	1	1	X <sup>2</sup>
$\bar{A}B$	X <sup>4</sup>	1	1	X <sup>6</sup>
$AB$	1 <sup>12</sup>	1 <sup>13</sup>	1 <sup>15</sup>	1 <sup>14</sup>
$A\bar{B}$	X <sup>8</sup>	1 <sup>9</sup>	1 <sup>11</sup>	X <sup>10</sup>

Q. Minimize the given function by using K-map.

$$Y = ABC + \bar{A}CD + A\bar{D}$$

$$Y = ABC(D + \bar{D}) + \bar{A}CD(B + \bar{B}) + A\bar{D} \{(B + \bar{B})(C + \bar{C})\}$$

$$= ABCD + ABC\bar{D} + \bar{ABC}D + \bar{ABC}\bar{C}D + ABC\bar{C}D + AB\bar{C}\bar{D}$$

$$= \bar{ABC}\bar{D} + ABC\bar{D} + \bar{ABC}D + \bar{ABC}\bar{C}D + ABC\bar{C}D + AB\bar{C}\bar{D} + \bar{ABC}\bar{C}\bar{D}$$

$$= 15, 14, 7, 3, 12, 10, 8$$

$$\text{So, } Y = \sum_m (3, 7, 8, 10, 12, 14, 15)$$

$AB\backslash CD$	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$	0	1	1	2
$\bar{A}B$	4	5	7	6
$AB$	12	13	15	14
$A\bar{B}$	8	9	11	10

Q. To run motor there are certain conditions:

- i) If switches A & C are closed but switch D is open, then motor will run.
- ii) If switches C & D are closed, other switches are open then motor will run.
- iii) If switches A & B are closed but switch D is open then motor will run.
- iv) If switch D is closed then we can't say motor will run or not.

## \* Flip-Flop :-

Flip-flop is a sequential circuit which stores the smallest unit of memory (i.e., data). It stores one bit data at a time. It is also known as bistable circuit.

There are 5 types of FF:-

- i) SR FF
- ii) JK FF
- iii) D FF
- iv) T FF
- v) Master Slave FF

## i) SR Flip-Flop :-


SR is the common flip-flop. It has two input signals (i.e S(set) and R(reset)). A flip-flop must have a special input signal called clock signal. The clock signal enable or disable the state change of the flip-flop.




DATE: \_\_\_/\_\_\_/\_\_\_

PAGE: \_\_\_

→ Block diagram :-

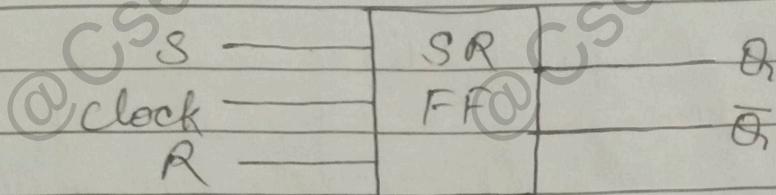

→ Main diagram :-

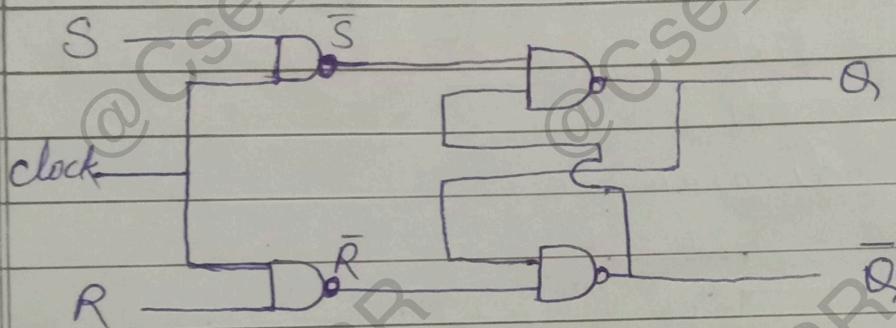

\* Characteristics function table / Table Truth Table

Clock	S	R	Q	$\bar{Q}$	Comment
0	x	x	Q	$\bar{Q}$	NC
1	0	0	Q	$\bar{Q}$	NC
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	?	?	Invalid




DATE: \_\_\_\_\_

PAGE: \_\_\_\_\_


## ii) JK Flip-Flop:-

JK flip-flop is the advance version of SR flip-flop. In SR FF, at  $S=1$ , and  $R=1$  and  $\text{clock} = 1$ , the system will give invalid condition. To overcome this problem JK FF has developed. In JK FF indeterminated condition of SR FF is defined in the JK FF. The input J and K behaves like input S and R respectively.

Block diagram:-

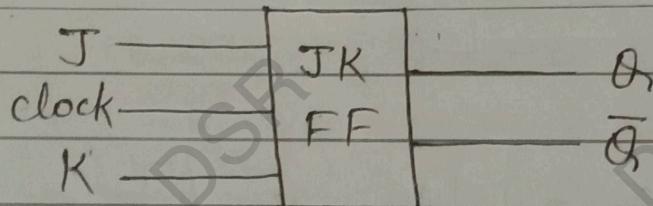

Main diagram :-

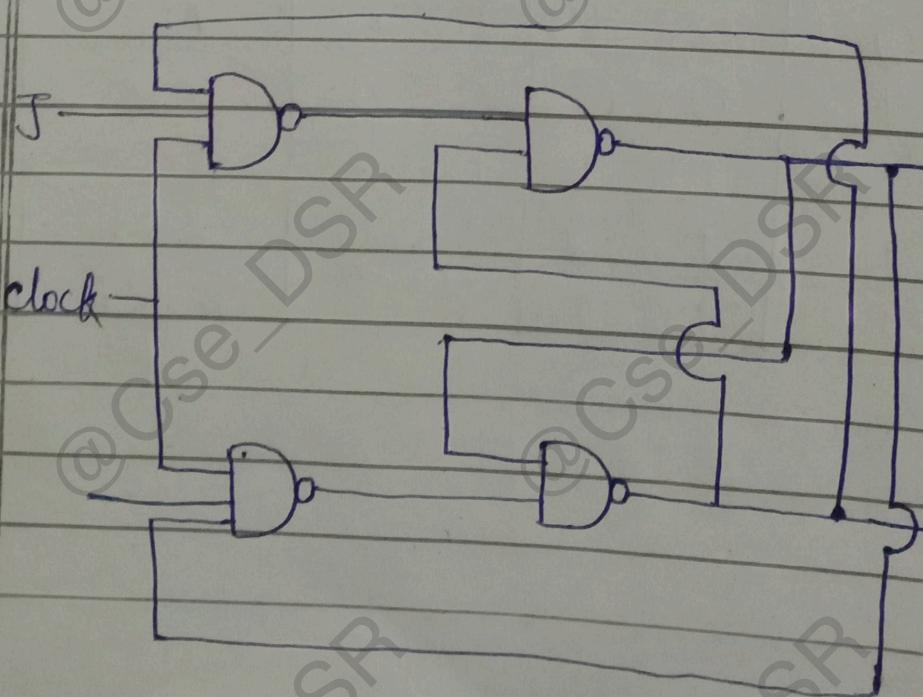


## Truth Table :-


Clock	S	R	Q	$\bar{Q}$	comment
0	X	X	0	0	NC
1	0	0	0	0	NC
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	0	0	Toggle

iii) D Flip-Flop:- D flip-flop is also known as data transfer flip-flop. It is a slight modification of SR flip-flop. And SR FF is converted to D FF by connecting R with NOT gate through S.


## Block diagram:-

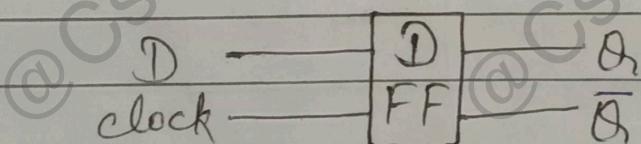

## DFF by using SR FF:-

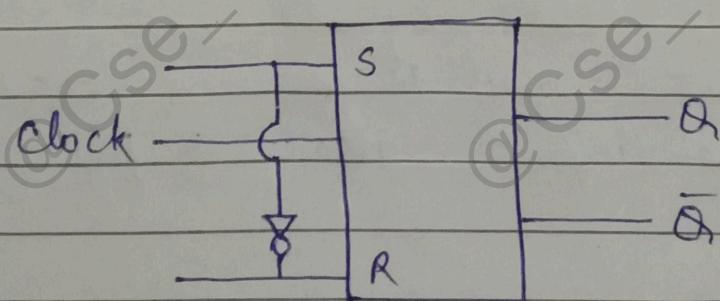

Main diagram & D FF using SR FF :-

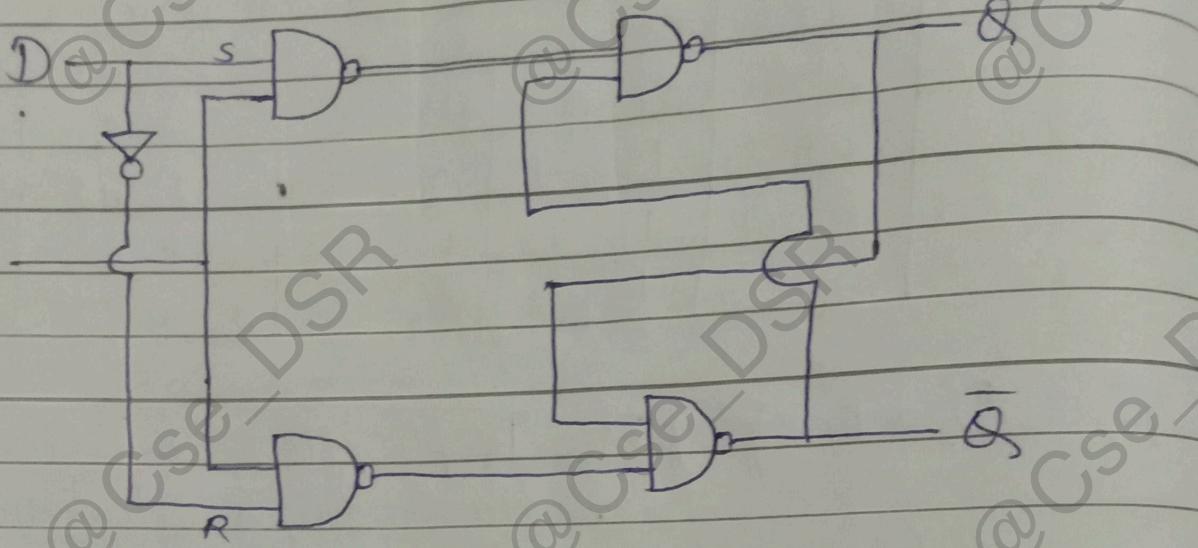



Truth Table

clock	D	Q	$\bar{Q}$	comment
0	X	Q	$\bar{Q}$	NC
1	0	0	1	reset
1	1	1	0	set


iv) T Flip-Flop :-

T flip-flop is known as toggle FF. This FF is made by J-K flip-flop, when input J and K are connected with single input called T flip-flop.

Block diagram :-

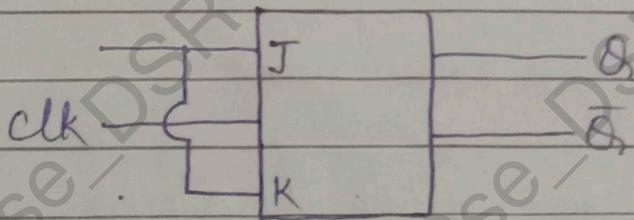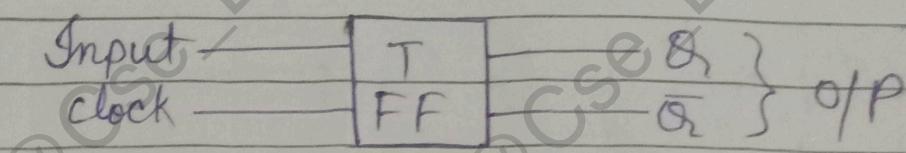

Main diagram:-

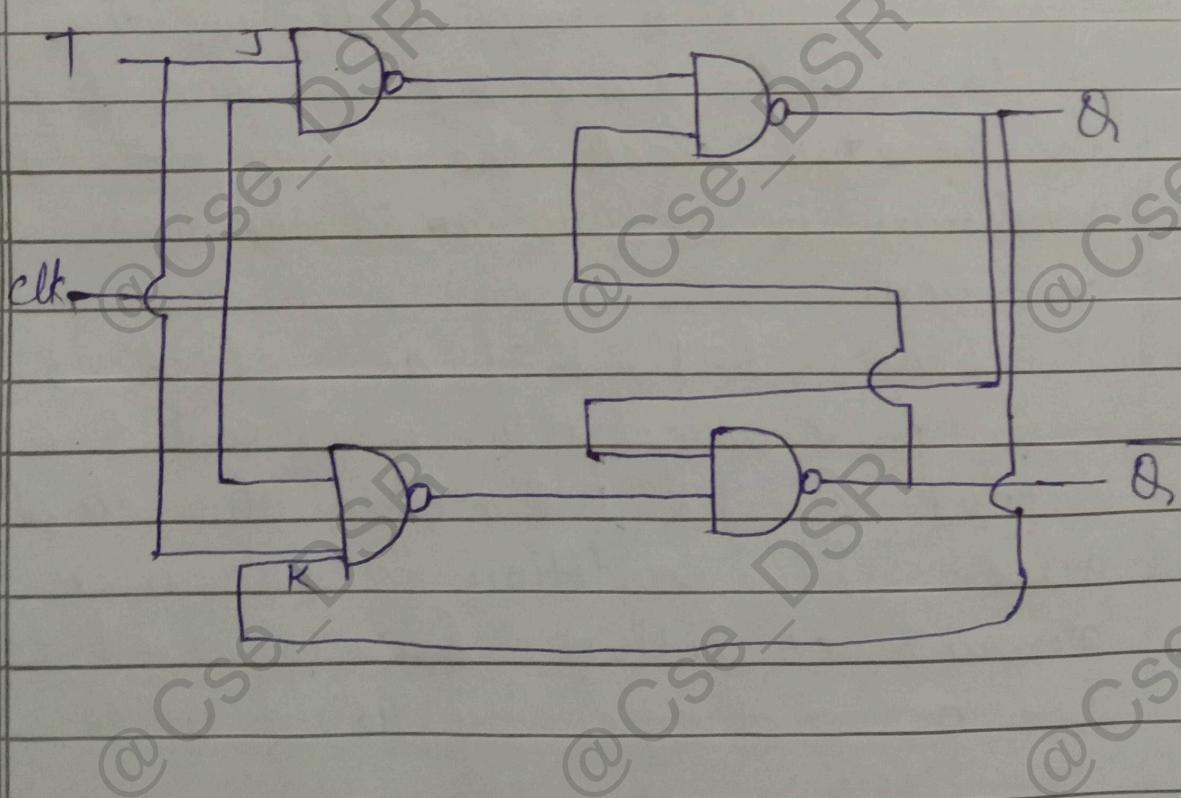

### Truth Table

Clock	T	$\bar{Q}$	$\bar{\bar{Q}}$	comment
0	X	0	0	NC
1	0	0	0	NC
1	1	0	0	toggle

v) Master Slave ~~statement~~ :-

Master slave flip-flop is another type of FF. In this FF, two FF are used, first is master FF, which respond to positive level of the clock. Second is slave FF, which respond to the negative level of the clock. Slave FF is connected to the inverted clock of the master FF. This condition is used to avoid the race around condition.

Where  $J=1$ ,  $K=1$  and clock = 1, then there is a race between 0 and 1 at the output of JK FF within the clock pulse. This condition is known as race around condition. Race around condition can be overcome by using master slave flip-flop.